

Chapter 2

COMBINATIONAL CIRCUITS

SMALL DESIGNS

Digital Logic Design and Computer Organization with Computer Architecture for Security 1

Signal Naming Standards

- Active-high signal polarity
 - 1 represents signal is active, asserted, enabled
 - 0, otherwise
 - E.g., signal labeled as x without a pre- or post symbol
- Active-low signal polarity
 - 0 represents signal is active, asserted, enabled
 - 1, otherwise
 - E.g., signal labeled as $_x, x', /x,$ or $x\#$
 - With a pre- or post-symbol

Digital Logic Design and Computer Organization with Computer Architecture for Security 4

In this Chapter

- Small Combinational Circuits
 - Fewer inputs (e.g., ≤ 4 inputs)
 - Circuits modeled as Truth Tables
 - Circuit minimization techniques
- Circuit implementation options
 - NANDs only
 - NORs only
- Timing diagram
 - Signal propagation delay
 - Understating signal hazards ("glitches")
- Other types of logic gates
- Design examples
- Introduction to design with HDL

Digital Logic Design and Computer Organization with Computer Architecture for Security 2

Primitive Logic Gates with Truth Tables

Digital Logic Design and Computer Organization with Computer Architecture for Security 5

Small Combinational Circuits

- Example: 2-bit unsigned multiplier, $P = A * B$
- Block diagram and truth table
 - Labeling of input and output signals
- Implementation options
 - LUT
 - Easier, slower, configurable
 - Logic circuit
 - Faster, less hardware

Digital Logic Design and Computer Organization with Computer Architecture for Security 3

SOP Expressions

- Based on input values that produce 1 as output
- Each such input is expressed as a product term
- Circuit performs AND-OR logic
 - Can be implemented with NAND gates
- DeMorgan's theorems convert AND-OR circuit into NAND-only circuit


Theorem 1: $\overline{\overline{x} + \overline{y}} = x + y$
 Theorem 2: $\overline{\overline{x} * \overline{y}} = x + y$

Digital Logic Design and Computer Organization with Computer Architecture for Security 6

POS Expressions

- Based on input values that produce 0 for f (an output)
 - Same input values produce 1 for \bar{f}
- Find expression for f by complementing \bar{f}
- Each such input is expressed as a sum term
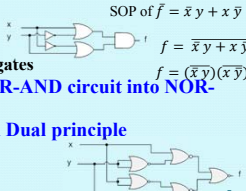
$$f = (x + \bar{y})(\bar{x} + y)$$
- Circuit performs OR-AND logic



SOP of $\bar{f} = \bar{x}y + x\bar{y}$

$f = \overline{\bar{x}y + x\bar{y}}$

$f = (\bar{x}\bar{y})(x\bar{y})$

 - Can be implemented with NOR gates
 - DeMorgan's theorems convert OR-AND circuit into NOR-only circuit
 - Also can use signal negation with Dual principle

$$\text{Dual of } \bar{f} = (\bar{x} + y)(x + \bar{y})$$

Digital Logic Design and Computer Organization with Computer Architecture for Security 7

Why minimize logic expressions

- Eliminates redundancies
- Requires fewer gates
- Fewer inputs per gates
- Less wire
- Less power usage
- Reduces circuit delay

How many gates and types for SOP?

Canonical SOP: 3 NOTs, four 3-input ANDs, one 4-input OR.

Minimal SOP: One NOT, two 2-input ANDs, one 2-input OR.

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Implement with NAND gates

Canonical SOP: $f = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xyz$

Minimal SOP: $f = \bar{x}z + xy$

Implement with NOR gates

Canonical POS: $f = (x + y + z)(\bar{x} + \bar{y} + z)(\bar{x} + y + z)(\bar{x} + y + \bar{z})$

Minimal POS: $f = (x + z)(\bar{x} + y)$

Digital Logic Design and Computer Organization with Computer Architecture for Security 10

Show mathematically

- NAND implementation

$f = \bar{f} \implies f = \overline{\bar{x}\bar{y} + x\bar{y}}$

Theorem 2

 $\xrightarrow{\bar{x} + \bar{y} = \bar{x}\bar{y}}$

 $f = \overline{(\bar{x}\bar{y})(x\bar{y})}$

NAND NAND

NAND, again
- NOR implementation

$f = (x + \bar{y})(\bar{x} + y) = \overline{\overline{(x + \bar{y})(\bar{x} + y)}} = \overline{\overline{(x + \bar{y})} + \overline{(\bar{x} + y)}}$

NOR NOR

NOR, again

Digital Logic Design and Computer Organization with Computer Architecture for Security 8

Karnaugh map (K-Map) Layouts

yz:	00	01	11	10
x: 0	0	1	3	2
1	4	5	7	6

2 x 4

z:	0	1
xy: 00	0	1
01	2	3
11	6	7
10	4	5

4 x 2

yz:	00	01	11	10
wx: 00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

4 x 4

Digital Logic Design and Computer Organization with Computer Architecture for Security 11

Canonical Expression

$g = x\bar{y} + \bar{x}z + xyz$ Non-Canonical

$g = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + x\bar{y}\bar{z} + xyz$ Canonical, every term has all the variable names

Min Terms vs. Canonical expression

For example, $g(x, y, z) = \sum(0, 1, 6, 7)$

$g(x, y, z) = \sum((000)2, (001)2, (110)2, (111)2)$

$g = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + x\bar{y}\bar{z} + xyz$

Inputs			Outputs			
x	y	z	$\bar{x}\bar{y}\bar{z}$	$\bar{x}\bar{y}z$	$x\bar{y}\bar{z}$	xyz
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1
1	0	0	0	0	1	0
1	0	1	0	0	0	1
1	1	0	0	0	0	1
1	1	1	0	0	0	1

$p2(a1, a0, b1, b0) = \sum(10, 11, 14)$

Digital Logic Design and Computer Organization with Computer Architecture for Security 9

SOP and POS K-maps

yz:	00	01	11	10
x: 0				1
1			1	1

$g(x, y, z) = \sum(2, 6, 7)$

SOP

yz:	00	01	11	10
x: 0	0	0	0	
1	0	0		

$g(x, y, z) = \Pi(0, 1, 3, 4, 5)$

POS

Digital Logic Design and Computer Organization with Computer Architecture for Security 12

Minimizing SOP Expressions

$\sum(2,3,6,7) = \bar{x}y\bar{z} + \bar{x}yz + xy\bar{z} + xyz$
 $= \bar{x}y(\bar{z} + z) + xy(\bar{z} + z)$ Factor out smaller terms and simplify
 $= \bar{x}y + xy$ Factor out y and simplify
 $= y(\bar{x} + x)$ Simplify
 $= y$

yz:	00	01	11	10
x:	0		1	1
	1		1	1

Each pair of adjacent terms reduces to a simplified expression with one less variable.

Digital Logic Design and Computer Organization with Computer Architecture for Security 13

Don't-Care Signal values

• Example: Displaying BCD numbers

A 7-segment display unit and converter

Inputs				Outputs						
w	x	y	z	fa	fb	fc	fd	fe	ff	fg
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	0	1	1
0	0	1	1	1	1	1	0	0	0	1
0	1	0	0	0	1	1	0	1	0	1
0	1	0	1	1	0	1	1	1	0	1
0	1	1	0	1	0	1	1	1	0	1
0	1	1	1	1	0	1	1	1	1	1
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	1	1	1
1	0	1	0							
1	0	1	1							
1	1	0	0							
1	1	0	1							
1	1	1	0							
1	1	1	1							

Assuming that w, x, y, and z will not exceed 9, what should we enter in the table for inputs 10 through 15?

Digital Logic Design and Computer Organization with Computer Architecture for Security 16

K-Map Minimization Rules

- 1) Min/max terms that differ in only one bit are adjacent (an **Implicant**). A K-map is assumed to wrap around on both sides.
- 2) A set of adjacent min/max terms may be combined to form a large group (a **Prime Implicant**). The number of terms in each group must be powers of 2
e.g., 2, 4, 8, or 16 terms.
- 3) Each group of min/max terms must contain at least a single term that doesn't belong to any other group (no redundant groups), an **Essential Prime Implicant**
- 4) All terms must be grouped.

Digital Logic Design and Computer Organization with Computer Architecture for Security 14

K-Map with Don't Cares

$f(w, x, y, z) = \sum(1, 9, 14) + \sum_d(3, 7, 11)$

	yz	00	01	11	10
wx	00	1	d		
	01		d		
	11			1	
	10	1	d		

$f(w, x, y, z) = \bar{x}z + wxy\bar{z}$

Digital Logic Design and Computer Organization with Computer Architecture for Security 17

More K-map Examples (no slides)

Digital Logic Design and Computer Organization with Computer Architecture for Security 15

Logic Minimization Algorithm

• Based on K-Map minimization technique

1. Compare neighboring min/max terms two at a time (e.g., 0000 with 0001) to produce all Implicants
2. Write the Implicant with a dash (e.g., 000-) for the bit that changes
3. Repeat steps 1 and 2 for neighboring terms with matching dashes (e.g., 000- with 100- to get -00-)
4. Prime implicants: Repeat step 3 until all prime implicants are identified
5. Essential prime implicants: Choose a minimum set among the prime implicants

Digital Logic Design and Computer Organization with Computer Architecture for Security 18

Minimization Software

$f(w, x, y, z) = \Sigma (0, 2, 3, 4, 5, 6, 7, 8, 10, 12, 13)$

Input File

```
#Inputs: 4, Outputs: 1
i 4
o 1
#Input labels
ilb w x y z
#Output bit label
ob f
#List of min-terms separated by space and a single output bit separated
by a tab
0 0 0 0 1
0 0 1 0 1
0 0 1 1 1
0 1 0 0 1
0 1 0 1 1
0 1 1 0 1
0 1 1 1 1
1 0 0 0 1
1 0 1 0 1
1 1 0 0 1
1 1 0 1 1
#end of list
.e
```

Output

```
#Inputs: 4, Outputs: 1
#Input signal labels
#Output bit label
#List of min-terms and output
#end of list
i 4
o 1
ilb w x y z
ob f
.p 3
-10-1
-4-0 1
0-1-1
.e
```

$\bar{x}z + \bar{w}y + xy$

• Can be used with don't care inputs too

Other Gates

- **Open collector (o.c.) buffer**
 - Application: Wired-logic with a large fan-in
 - E.g., wired-AND or wired-OR logic
 - Many application areas
- **Tri-state buffer**
 - Used to create a bus for multiple modules to transmit data
 - Modules not outputting to the bus should be electrically isolated

e	In	Out
0	0	Z
0	1	Z
1	0	0
1	1	1

Circuit Timing Diagram

1. Circuits have gate and signal wire delays
2. Gates may have different output signal rise and fall times
3. Circuits have different signal paths from inputs to outputs

- These may result in signals reaching each gate at different times
- Can cause unwanted signal change (glitch) at some outputs
- Must wait for the longest signal propagation delay before the output(s) of a circuit can be used (e.g., stored in a register)

Small combinational design examples

- **Full-adder circuit**
- **Multiplexer circuit**
 - Selects data one from 2 or more inputs
- **Decoder circuit**
 - Translates an input value to a corresponding signal
- **Encoder circuit**
 - Translates an active input signal to a corresponding signal number

Circuit Fan-In and Fan-Out

- **Fan-in:** Number of gate inputs
- **Fan-out:** Number of places a gate output can connect to
- **Buffer gate to increase a gate's fan-out**


Logic Implementation

- ASIC (application specific integrated chip)
- FPGA (Field Programmable Gate Arrays)

Altera FPGA board

FPGA internal

 CLB	 Interconnection switch block	 I/O block	 Wiring channel
---	---	--	---

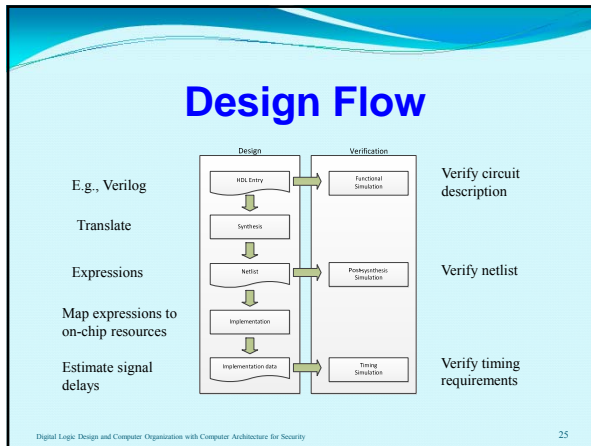

Behavioral Model

```


module full_adder
(
    input a, b, cin,
    output reg s, cout
);
always@(a or b or cin)
begin
    case (a, b, cin)
        3'b000: begin s = 0, cout = 0, end
        3'b001: begin s = 1, cout = 0, end
        3'b010: begin s = 1, cout = 0, end
        3'b011: begin s = 0, cout = 1, end
        3'b100: begin s = 1, cout = 0, end
        3'b101: begin s = 0, cout = 1, end
        3'b110: begin s = 0, cout = 1, end
        3'b111: begin s = 1, cout = 1, end
        default: begin s = 0, cout = 0, end
    endcase
end
endmodule
    
```

Digital Logic Design and Computer Organization with Computer Architecture for Security 28

Design Entry

- Schematic entry
- Hardware Description Language
- **Structural Model**
 - Use gates
 - Use predefined modules
- **Behavior model**
 - Use Boolean expressions, if-else, case (switch), for-loop, operators "+, -, *, /", etc.
 - Not all behavioral models are synthesizable
 - Applications of non-synthesizable models
 - Generate test vectors for synthesizable models
 - Investigate computer architecture design ideas
- **Hybrid**
 - Use both structural and behavioral models

Schematic Entry

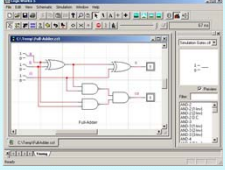

Digital Logic Design and Computer Organization with Computer Architecture for Security 26

A summary of Verilog HDL operators

Precedence	Operator Type	Symbol	Example
Highest	Unary	+, -, !, ~	+a, -a (negate a), !a (logical not), ~a (bitwise not)
	Exponential	**	a ** b (a cubed)
	Arithmetic 1	*, /, %	a * b (multiply), a / b (divide), a % b (mod)
	Arithmetic 2	+, -	a + b (add), a - b (subtract)
	Shift:		
	Logical	<<, >>	a << 2 (shift left twice)
	Arithmetic	<<<, >>>	a >>> 3 (shift right 3 times extending the sign bit)
	Relational	<, <=, >, >=	a >= b (a greater or equal to b)
	Equality		
	Logical	==, !=	a == b if a is identical to b excluding x and z
	Case	===, !==	a === b is identical to b including x and z
	Bit-wise		
	Basics	&, , ~, ^	a & b (and), a b (or), ~a (not), a ^ b (xor)
	Combined	&~, ~, ~^, ^~	a &~ b (nand), a ~ b (nor), a ^~ b (xnor), a ~^ b (xnor)
	Logical	&&, , !	a && b (and), a b (or), !a (not)
Lowest	Conditional	?:	(a >= b) ? a - b : b - a

Digital Logic Design and Computer Organization with Computer Architecture for Security 29

Structural Model Using Primitive Gates


```

module full_adder
(
    input a, b, cin,
    output s, cout
); //defines a module's name and its interface signals

    wire out1, out2, out3; //defines local signal names

    xor x1(out1, a, b);
    xor x2(s, out1, cin);
    nand n1(out2, out1, cin);
    nand n2(out3, a, b);
    nand n3(cout, out2, out3);

endmodule
    
```

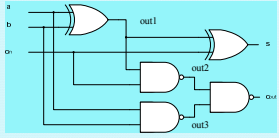

Digital Logic Design and Computer Organization with Computer Architecture for Security 27